

Name:

Honor Code:





KEY

Instructions:

- Use the space on the accompanying pages to work the problems. Do not use a bluebook. Attach additional worksheets if necessary. Label additional sheets with your name.
- If you wish to have partial credit awarded for any of your incorrect answers you must write clearly and legibly. Explain your work in words, if necessary.
- Write and sign the honor code when you are finished.
- Don't Panic.

Good Luck.

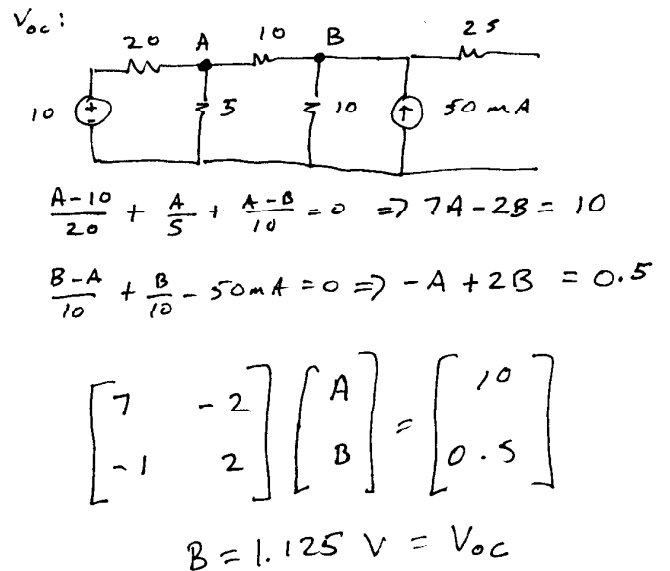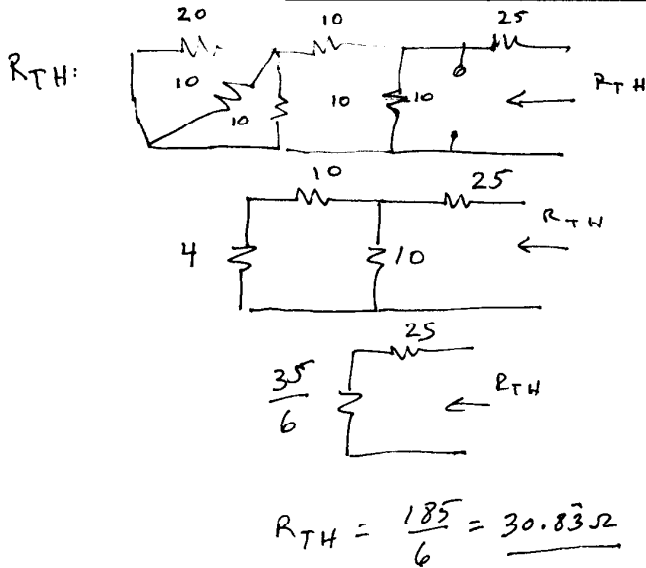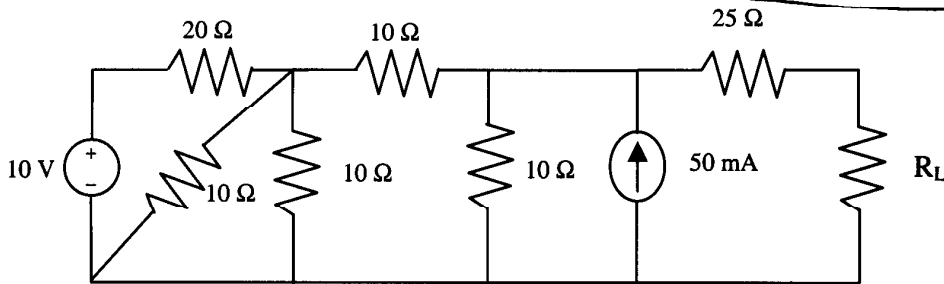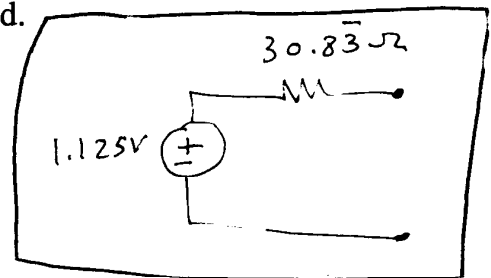
1. [25] Find the Thevenin equivalent circuit for the following.



2. [30] For the following circuit:

a. [10] Find  $I_0$ .

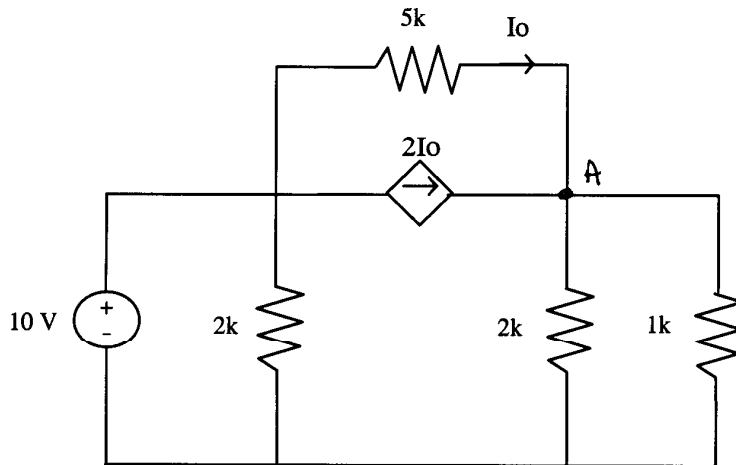b. [20] Show that the sum of the power absorbed/supplied by the circuit is 0.



a) Nodal @ A:  $-I_0 - 2I_0 + \frac{A}{2000} + \frac{A}{1000} = 0$

$$-6000 I_0 + 3A = 0$$

$$A = 2000 I_0$$

$$I_0 = \frac{10 - A}{5000}$$

$$A = 10 - 5000 I_0$$

$$2000 I_0 = 10 - 5000 I_0, \quad I_0 = \frac{10}{7} \text{ mA}$$

b)  $A = 2000 I_0 = 2000 \left( \frac{10}{7} \text{ mA} \right) = \frac{20}{7} \text{ V}$

Powers:


- 5K resistor :  $P = V^2/R = (10 - 20/7)^2 / 5000 = +10.20 \text{ mW}$
- 2K on right :  $P = V^2/R = (20/7)^2 / 2000 = +4.08 \text{ mW}$
- 1K resistor :  $P = V^2/R = (20/7)^2 / 1000 = +8.16 \text{ mW}$
- 2k on left :  $P = V^2/R = 10^2 / 2000 = +50 \text{ mW}$
- $2I_0$  source :  $P = IV = (2 \cdot 10/7 \text{ mA}) \left( 10 - \frac{20}{7} \right) = +20.40 \text{ mW}$
- 10V source :  $P = IV = \left( 3I_0 + \frac{10}{2000} \right) (10)$

3

$$= \left( 3 \cdot \frac{10}{7} \text{ mA} + \frac{10}{2000} \right) (10) = -92.85 \text{ mW}$$

0 ✓

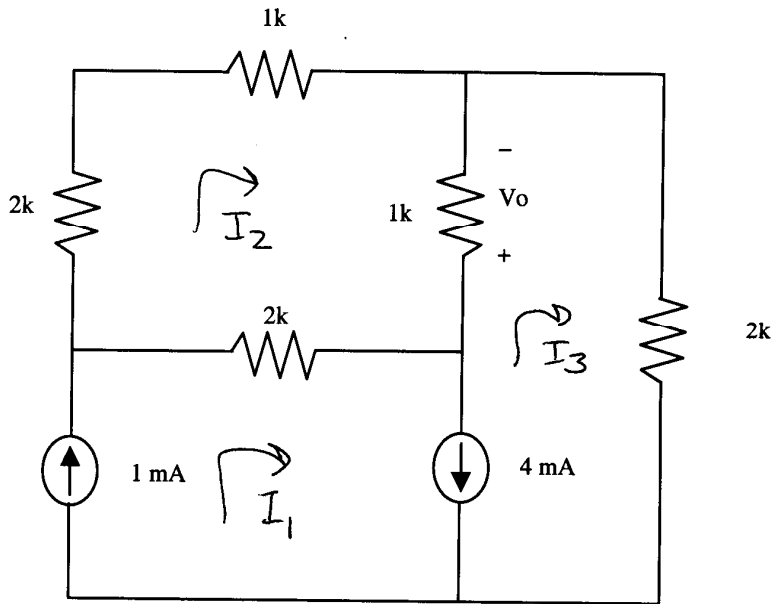3. [15] Find  $V_o$  in the following circuit.



$$\underline{I_1 = 1 \text{ mA}}$$

$$I_1 - I_3 = 4 \text{ mA}, \quad \underline{I_3 = -3 \text{ mA}}$$

$$2000 I_2 + 1000 I_2 + 1000 (I_2 - I_3) + 2000 (I_2 - I_1) = 0$$


$$-2000 I_1 + 6000 I_2 - 1000 I_3 = 0$$

$$I_2 = \frac{1}{6000} (2000 I_1 + 1000 I_3)$$

$$= \frac{1}{6000} (2 - 3) = \underline{-\frac{1}{6} \text{ mA}}$$

$$V_o = 1000 (I_3 - I_2) = 1000 (-3 + \frac{1}{6}) = \underline{\underline{-2.833 \text{ V}}}$$

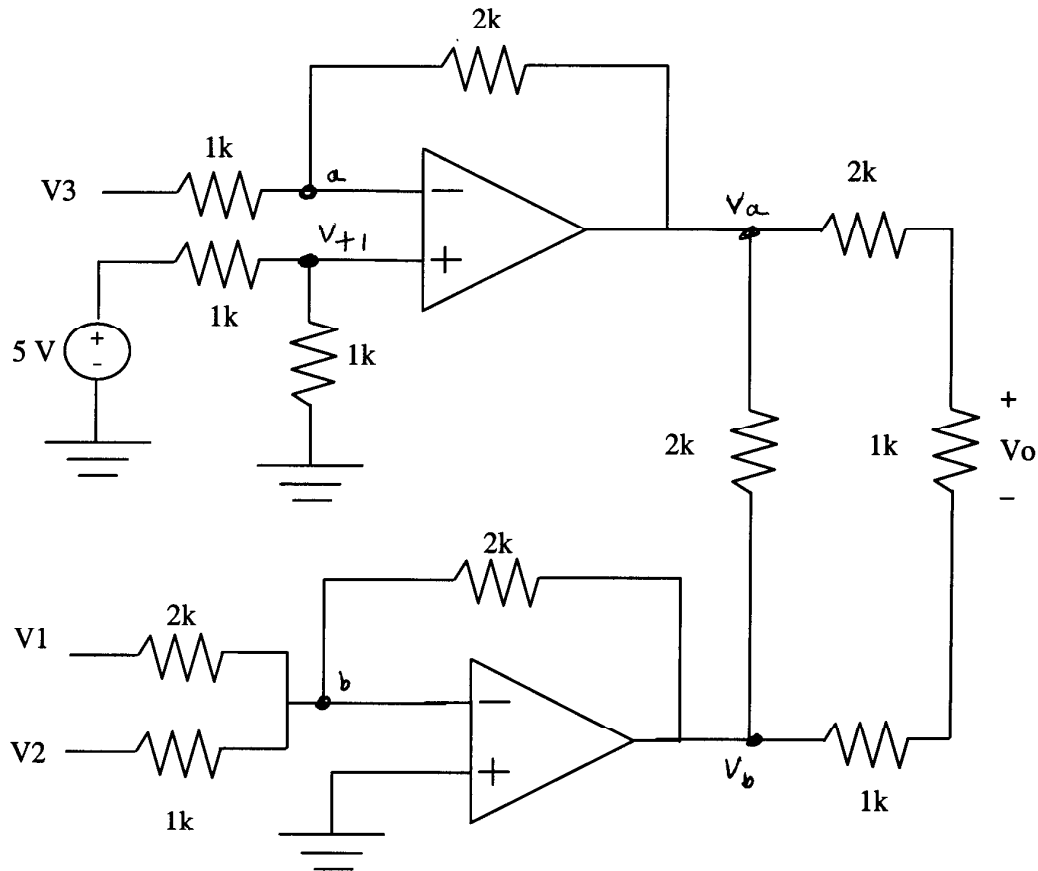4. [30] Find  $V_o$  as a function of  $V_1$ ,  $V_2$ , and  $V_3$  in the following circuit.



Top opamp:

$$V_{+1} = 5 \times \left( \frac{1000}{1000+1000} \right) = 2.5 \text{ V} \quad (\text{Voltage Divider})$$


$$\text{nodal at } a: \quad \frac{a - V_3}{1000} + \frac{a - V_a}{2000} = 0, \quad \text{but } a = 2.5 \text{ V}$$

$$\text{so } \underline{V_a = 7.5 - 2V_3}$$

bottom opamp:

$$\text{Inverting adder } \underline{V_b = -V_1 - 2V_2}$$
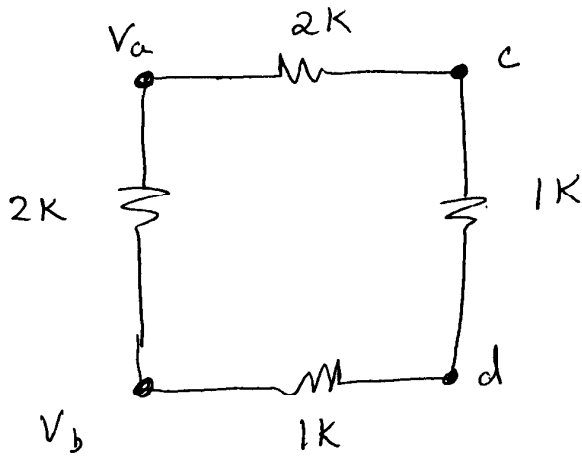
$$(\text{nodal at } b: \quad \frac{b - V_1}{2000} + \frac{b - V_2}{1000} + \frac{b - V_b}{2000} = 0) \quad (\text{cont.})$$



nodal at c  $\frac{c - V_a}{2000} + \frac{c - d}{1000} = 0$

$$\underline{3c - 2d = V_a}$$

nodal at d  $\frac{d - c}{1000} + \frac{d - V_b}{1000} = 0$

$$\underline{-c + 2d = V_b}$$

add equations  $2c = V_a + V_b$   
 $c = \frac{V_a + V_b}{2}$

$$d = \frac{V_b + c}{2} = \frac{V_b + \frac{1}{2}V_a + \frac{1}{2}V_b}{2}$$

$$= \frac{3V_b + V_a}{4}$$

$$V_o = c - d = \frac{V_a + V_b}{2} - \frac{3V_b + V_a}{4} = \frac{V_a - V_b}{4}$$

$$= \frac{7.5 - 2V_3 + V_1 + 2V_2}{8}$$